

Indian Institute of Technology (IIT-Kharagpur)

AUTUMN Semester, 2025 COMPUTER SCIENCE AND ENGINEERING (COA Laboratory)

Introduction to Verilog Programming

In this assignment, we shall be designing and comparing two adder circuits using the Verilog Programming Language. The first part of the assignment is on the design of the Ripple Carry Adder (RCA) and Carry Look-ahead Adder (CLA), which is a faster adder.

1. The first problem is on the design of a RCA. Write the Verilog Code for an n -bit adder. Proceed step by step as follows:
 - (a) A **Half Adder** is a combinational circuit, which takes in two input bits, a and b , and produces the sum bit, s and the carry-out bit, c . Write the truth-table for the assignments of s and c . Write the verilog code for the **Half Adder**.
 - (b) A **Full Adder** is a combinational circuit, which takes in three input bits, a , b , and in addition a carry-in bit c_0 , and produces the sum bit, s and the carry-out bit, c . Write the truth-table for the assignments of s and c in the Full-Adder. Write the verilog code for the **Full Adder**.
 - (c) Cascade 8 Full adders and create an 8-bit adder. These type of adders are called **Ripple Carry Adders**. Like-wise create, 16, 32, and 64 bit adders.
 - (d) How can you use the above circuit, to compute the difference between two n -bit numbers?
2. In the previous assignment, we have designed a Ripple Carry Adder (RCA). One of the weaknesses in the adder is the large delay because of the rippling of the carry, through what we call as the carry-chain. In this assignment, we endeavour to design a high-speed adder using the technique of what we call as the Carry Look-ahead Adder (CLA). In this exercise, we start with designing a 4-bit CLA and then use it to design a 16-bit CLA using a hierarchical structure.

Proceed as follows:

- (a) First, design a 4-bit CLA. Clearly state, the Boolean equations of the Look-ahead carry generation for the 4 carry bits, C_1 , C_2 , C_3 , and C_4 in terms of the generate and propagate signals, denoted as G_0, \dots, G_3 and P_0, \dots, P_3 respectively. Also state the equations for the corresponding generate and propagate signals.

- (b) Now let us try to make a 16-bit adder in a *hierarchical* fashion. For this, we observe that $C4 = G3 + P3G2 + P3P2G1 + P3P2P1G0 + P3P2P1P0C0$. One can create the 16-bit adder in two ways. In both the ways, we reuse the 4-bit CLA just designed by you. However, in one of the ways we ripple in the carry out from the 4-bit CLA to the second stage, while in the other we compute the carry in of the second 4-bit CLA by using a separate level of Lookahead Carry Unit. This lookahead carry unit works on block propagates and block generates, denoted as P, G in the circuit shown in **Fig 1**. The definitions of the block propagate and block generate are as follows:

$$P = P3P2P1P0 \quad (1)$$

$$G = G3 + P3G2 + P3P2G1 + P3P2P1G0 \quad (2)$$

Thus, we can write $C4 = G + PC0$. Now if you consider wrt. the Lookahead Carry Unit, this is the logic for the carry bit C1. Likewise, one can compute the logic for the carry bits, C2, C3, and C4 using the block propagates and generates. We also compute P3-0 and G3-0 which are block propagates and generates for the next level of the hierarchy (if one wishes to design 32 or 64 bit adders using this structure as a component). *Note that the labels for the propagates and generates can be confusing, but since the labels are written internal to the blocks (or verilog modules) they dont conflict with each other.* In this part you are supposed to:

- Augment the 4-bit adder to compute the block propagate and generate signals. Test the circuit using a testbench in verilog.
- Design the Lookahead Carry Unit and integrate as shown in **Fig 1**.

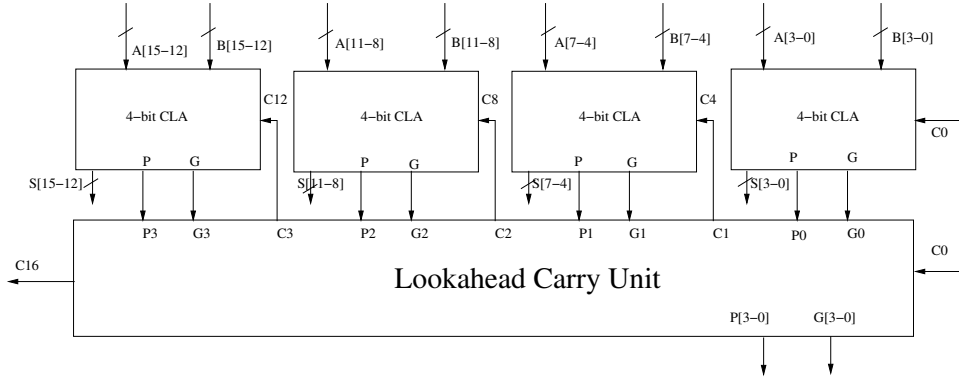


Figure 1: The Hierarchical Structure of a 16-bit CLA